

Basavarajeswari Group of Institutions

BALLARI INSTITUTE OF TECHNOLOGY & MANAGEMENT
 (Autonomous Institute under Visvesvaraya Technological University, Belagavi)

2022 SCHEME

USN

Course Code 2 2 B E E 13 / 23

First/Second Semester B.E. Degree Summer Semester Examinations, September/October 2025

BASIC ELECTRONICS

Duration: 3 hrs

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
 2. Missing data, if any, may be suitably assumed.

<u>Q. No</u>	<u>Question</u>	<u>Marks</u>	<u>(RBTL:CO:PI)</u>
<u>Module-1</u>			
1.	a. With a neat circuit diagram and waveform, explain the operation of full-wave centre-tapped rectifier.	06	(2:1:1.3.1)
	b. With relevant equations explain DC-load line analysis of a diode.	06	(2:1:1.3.1)
	c. What is PN junction? Explain PN junction diode under forward biased and reverse biased condition.	08	(2:1:1.3.1)
(OR)			
2.	a. Explain the working of DC power supply with a neat block diagram.	06	(2:1:1.3.1)
	b. Explain how Zener diode can be used as a voltage regulator with a load.	06	(2:1:1.3.1)
	c. Describe the working of a RC- π filter for a full wave rectifier with neat diagram and necessary waveforms.	08	(2:1:1.3.1)
<u>Module-2</u>			
3.	a. List out the difference between Common Emitter (CE), Common Collector (CB), and Common Collector (CC) configuration modes of a transistors.	06	(2:2:1.3.1)
	b. Explain Common Emitter configuration of NPN transistor with a neat diagram.	06	(2:2:1.3.1)
	c. Define BJT. Give Symbol and layer diagram of NPN and PNP Transistor with its terminal voltages and currents.	08	(2:2:1.3.1)
(OR)			
4.	a. Define FET. List out the difference between BJT and FET.	06	(2:2:1.3.1)
	b. Explain n-channel FET with a neat diagram.	06	(2:2:1.3.1)
	c. Explain the working of enhancement mode of n-channel FET along with its characteristics.	08	(2:2:1.3.1)
<u>Module-3</u>			
5.	a. Define Op-Amp. Give the symbol and pin diagram of the same.	06	(2:3:1.3.1)
	b. List and explain the ideal characteristics of OP-AMP.	06	(2:3:1.3.1)
	c. Derive the output voltage equation of an inverting amplifier and non-inverting amplifier.	08	(2:3:1.3.1)

(OR)

6. a. Explain how OP-AMP can be used as a voltage follower with a neat wave form. 06 (2:3:1.3.1)
 b. Explain how OP-AMP can be used as a comparator. 06 (2:3:1.3.1)
 c. Explain how OP-AMP can be used as an integrator and differentiator with a neat wave form. 08 (2:3:1.3.1)

Module-4

7. a. Convert following: (i) $76.57_{(8)}$ into $\text{_____}_{(16)}$ (ii) $D5.A_{(16)}$ into $\text{_____}_{(8)}$ 06 (2:4:1.3.1)
 b. State and prove Demorgan's theorems. 06 (2:4:1.3.1)
 c. Convert the following into Canonical forms: 08 (2:4:1.3.1)
 (i) $f(A,B,C) = AC + AB + BC$ (ii) $F(A,B,C) = (A+B).(B+C).(A+C)$

(OR)

8. a. Define SOP and POS, and write the minterm and Maxterm for the given truth table. 06 (2:4:1.3.1)

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

- b. Draw the symbols and truth table and equation for all logic gates. 06 (2:4:1.3.1)
 c. Design and draw full-adder circuit using logic gates. 08 (2:4:1.3.1)

Module-5

9. a. Define embedded system. With a neat block diagram, explain elements of an embedded System. 06 (2:5:1.3.1)
 b. Explain the classification of embedded system with a neat diagram. 06 (2:5:1.3.1)
 c. List the difference between embedded systems Vs general computing system. 08 (2:5:1.3.1)

(OR)

10. a. List out the difference between microprocessor Vs microcontroller. 06 (2:5:1.3.1)
 b. Explain the block diagram of general communication system. 06 (2:5:1.3.1)
 c. Explain the different types of modulation techniques with neat wave forms. 08 (2:5:1.3.1)

** ** *