

USN

--	--	--	--	--	--	--	--	--	--

Course Code

2	2	E	E	E	13	/	23
---	---	---	---	---	----	---	----


First/Second Semester B.E. Degree Summer Semester Examinations, September/October 2025

ELEMENTS OF ELECTRICAL ENGINEERING

Duration: 3 hrs

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
2. Missing data, if any, may be suitably assumed.
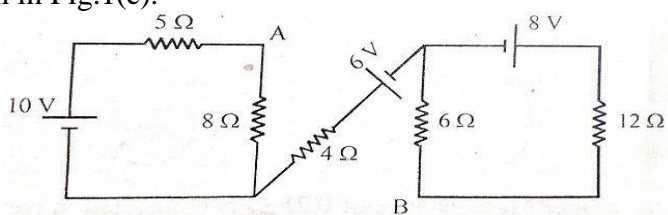
<u>Q. No</u>	<u>Question</u>	<u>Marks</u>	<u>(RBTL:CO:PI)</u>
<u>Module-1</u>			
1.	a. State and explain Kirchhoff's laws.	06	(2:1:1.3.1)
	b. A current of 10 A flows through two ammeters A and B connected in series. The potential differences across A and B are 0.2 V and 0.3 V respectively. Find how the same current will divide between A and B when they are connected in parallel.	07	(2:1:1.3.1)
	c. Find the potential difference between the points A and B in the network shown in Fig.1(c).	07	(3:1:2.1.2)
 <p style="text-align: right;">Fig.1(c)</p>			
(OR)			
2.	a. State and explain Faraday's laws of electromagnetic induction.	06	(2:1:1.3.1)
	b. Define coefficient of coupling and derive an expression for it.	07	(2:1:1.3.1)
	c. Two identical coils of 1200 turns each are placed side by side such that 60 % of the flux produced by one coil links the other. A current of 10 A in the first coil sets up a flux of 0.12 mWb. If the current in the first coil changes from +10 A to -10 A in 20 mS. Find (i) the self-inductances of the coils (ii) the e.m.f induced in both the coils.	07	(3:1:2.1.2)
<u>Module-2</u>			
3.	a. Define average value of sinusoidal varying current and derive an expression for its maximum value.	06	(2:2:1.3.1)
	b. With necessary circuit diagram and wave forms prove that the power drawn by the pure inductance in ac circuit is zero.	07	(2:2:1.3.1)
	c. Three alternating voltages $v_1=141 \sin(\omega t+\pi/4)$, $v_2=30 \sin(\omega t+\pi/2)$ & $v_3=20 \sin(\omega t - \pi/6)$ are fed into a common conductor. Find the equation for the resultant voltage, its rms value, form factor & peak factor.	07	(3:2:2.1.2)
(OR)			
4.	a. Using power triangle, define and explain the different types of power in 1-Ø AC system.	06	(2:2:1.3.1)
	b. An inductive coil takes a current of 33.24 A from 230 V, 50 Hz supply. If the resistance of the coil is 6 Ω. Calculate the inductance of the coil and power taken by the coil.	07	(2:2:1.3.1)

- c. Two impedances $(150 - j 157) \Omega$ and $(100 + j 110) \Omega$ are connected in parallel across 200 V, 50 Hz supply. Find the branch currents, total current and total power consumed in the circuit **07 (3:2:2.1.2)**

Module-3

5. a. What are the advantages of 3- \emptyset system over 1- \emptyset system? **06 (2:3:1.3.1)**
 b. Find the relation between the phase and line quantities of voltage and current for a 3- \emptyset star connection and deduce the power equation from the same. **07 (2:3:1.3.1)**
 c. A delta connected load consists of a resistance of 10Ω and a capacitance of $100 \mu\text{F}$ in each phase. A supply of 410 V at 50 Hz is applied to the load. Find the line current, power factor and power consumed by the load. **07 (3:3:2.1.2)**

(OR)

6. a. Briefly explain block diagram and functionality of Trivector meter. **06 (2:3:1.3.1)**
 b. Find the relation between the phase and line quantities of voltage and current for a 3- \emptyset delta connection and deduce the power equation from the same. **07 (2:3:1.3.1)**
 c. Three coils each having a resistance of 10Ω and an inductance of 0.02 H are connected in star across 440V, 50 Hz, three phase supply. Calculate the line current and power consumed by the circuit. **07 (3:3:2.1.2)**

Module-4

7. a. With a neat circuit diagram explain the working of Whetstone bridge and derive its equation for balanced condition. **06 (2:4:1.3.1)**
 b. Write a short note on Megger. **07 (2:4:1.3.1)**
 c. Mention the various types of domestic wiring and with a neat diagram explain casing and capping type of wiring. **07 (2:4:1.3.1)**

(OR)

8. a. With a neat diagram and switching table, explain two way control of lamp. **06 (2:4:1.3.1)**
 b. With a neat circuit diagram explain the working of Schering bridge and derive its equation for balanced condition. **07 (2:4:1.3.1)**
 c. Write a short note on (i) Current transformer and (ii) Potential transformer. **07 (2:4:1.3.1)**

Module-5

9. a. Write a short note on (i) MCB (ii) Fuse **06 (2:5:1.3.1)**
 b. Define a UNIT. Explain the concept of two part tariff. **07 (2:5:1.3.1)**
 c. What is the necessity of earthing? Explain the method of pipe earthing with a neat diagram. **07 (2:5:1.3.1)**

(OR)

10. a. Write a short note on (i) RCCB (ii) ELCB **06 (2:5:1.3.1)**
 b. What are the safety precautions to be taken while working with electricity to avoid shocks? **07 (2:5:1.3.1)**
 c. The domestic power load in a house comprises 8 lamps of 100 W each, 3 fans of 80 W each, 1 refrigerator of $\frac{1}{2}$ HP and one electric heater of 1kW. Calculate (i) Current drawn from 230 V supply (ii) Energy consumed in a day, if on an average only a quarter of the load is present all the time. **07 (2:5:1.3.1)**

** ** *