

Basavarajeswari Group of Institutions

BALLARI INSTITUTE OF TECHNOLOGY & MANAGEMENT
 (Autonomous Institute under Visvesvaraya Technological University, Belagavi)

2022 SCHEME

USN

Course Code 2 2 E S C 2 4 3

Second Semester B.E. Degree Summer Semester Examinations, September/October 2025

INTRODUCTION TO ELECTRONICS ENGINEERING

Duration: 3 hrs

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
 2. Missing data, if any, may be suitably assumed.

<u>Q. No</u>	<u>Question</u>	<u>Marks</u>	<u>(RBTL:CO:PI)</u>
<u>MODULE – 1</u>			
1.	a. Explain how Zener diode can be used as a voltage regulator.	08	(2:1:1.1.1)
	b. Explain the working of DC power supply with a neat block diagram.	08	(2:1:1.1.1)
	c. Define rectifier. With a neat circuit diagram and waveform, explain half-wave rectifier with a filter.	04	(3:1:1.2.1)
(OR)			
2.	a. Explain the role of R, L and C components in electronic circuit.	08	(2:1:1.1.1)
	b. Explain the operation of centre tapped full wave rectifier with neat circuit diagram, waveforms and mention its drawback.	08	(2:1:1.1.1)
	c. With the VI characteristics curve, explain the operation of PN junction under no bias, forward biased and reverse biased condition.	04	(3:1:1.2.1)
<u>MODULE – 2</u>			
3.	a. Explain negative feedback amplifier. Derive the voltage gain equation for negative feedback amplifier.	08	(2:2:1.1.1)
	b. With a circuit diagram and relevant equations, explain wein bridge oscillator.	08	(2:2:1.1.1)
	c. List and explain the ideal characteristics of OPAMP.	04	(3:2:1.2.1)
(OR)			
4.	a. List and explain the different types of amplifiers.	08	(2:2:1.1.1)
	b. Explain the Barkhausen's criteria for oscillations.	08	(2:2:1.1.1)
	c. Derive an expression for output voltage of an OPAMP integrator and differentiator.	04	(3:2:1.2.1)
<u>MODULE – 3</u>			
5.	a. Convert the following	08	(2:3:1.1.1)
	(i) $(FA876)_{16} = (?)_2 = (?)_{10} = (?)_8$		
	(ii) $(9734)_{10} = (?)_2 = (?)_{16} = (?)_8$		

	b.	Define shift register. Explain SIPO shift register.	08	(2:3:1.1.1)
	c.	Explain full adder. Implement full adder using 2 half adder and an OR gate.	04	(3:3:1.2.1)
		(OR)		
6.	a.	Simplify the following Expression	08	(2:3:1.1.1)
	(i)	$\overline{AB} + \bar{A} + AB$		
	(ii)	$AB + ABC + \bar{A}B + A\bar{B}C$		
	b.	State and prove De-morgans theorem of 2 variables.	08	(2:3:1.1.1)
	c.	Define sequential logical circuit. Explain clocked SR flip-flop using neat circuit diagram and truth table.	04	(3:3:1.2.1)
		MODULE – 4		
7.	a.	List the differences between microprocessor and microcontroller.	05	(2:4:1.1.1)
	b.	List the differences between RISC and CISC.	05	(2:4:1.1.1)
	c.	Explain the classification of embedded systems.	10	(3:5:1.2.1)
		(OR)		
8.	a.	With a neat block diagram explain the elements of an embedded system.	05	(1:4:1.1.1)
	b.	Explain the different configurations of the 7-segment LED display.	05	(2:4:1.1.1)
	c.	Compare embedded systems and general computing systems. Also provide major application areas of embedded system.	10	(3:5: .1.3)
		MODULE – 5		
9.	a.	Describe the blocks of basic communication system with neat block diagram.	05	(2:4:1.1.1)
	b.	Define frequency modulation. With the help of wave forms, explain frequency modulation.	05	(2:4:1.1.1)
	c.	With neat diagram, explain the concept of ground, space, sky radio wave propagation.	10	(3:5:2.1.3)
		(OR)		
10.	a.	List out the advantages of digital communication over analog communication.	05	(3:4:1.1.1)
	b.	Define amplitude modulation. With the help of waveforms, explain amplitude modulation.	05	(2:4:1.1.1)
	c.	Explain the concept of ASK, FSK and PSK with wave forms.	10	(3:5:2.1.3)
