

USN

--	--	--	--	--	--	--	--	--	--

Course Code

2	1	E	C	6	3
---	---	---	---	---	---

Sixth Semester B.E. Degree Examinations – September 2024
FUNDAMENTALS OF VLSI DESIGN

Duration: 3 hrs

Max. Marks: 100

Note: 1. Answer any FIVE full questions choosing ONE full Question from each Module.
 2. Missing data, if any, may be suitably assumed

<u>Q. No</u>	<u>Question</u>	<u>Marks</u>	<u>(RBTL:CO:PO)</u>
Module-1			
1.	a. Explain the following non ideal effects of MOS device 1. Channel length modulation 2. Body effect.	6	2:1:1.6.1
	b. What is a noise margin? Obtain the values of VIL, VOL, VIH and VOH from transfer characteristics of a typical inverter.	6	2:1:1.6.1
	c. Explain the ideal IV characteristics of nMOS transistor. Derive the equation for ID _S Cut off, Linear and Saturation region	8	2:1:1.6.1
OR			
2.	a. With neat diagram, explain the nMOS fabrication steps.	6	2:1:1.6.1
	b. Compare Bipolar and CMOS technology.	6	2:1:1.6.1
	c. Explain the CMOS inverter transfer characteristics by highlighting the regions of the MOS transistor.	8	2:1:1.6.1
Module-2			
3.	a. Explain with circuit diagram the super buffers with inverting type and non-inverting type of nMOS.	6	2:1:1.6.1
	b. Draw the schematic, stick diagram and Layout for 2 input CMOS NOR gate.	6	2:2:1.6.1
	c. Derive expressions for rise time and fall time for 1:1 CMOS inverter.	8	3:1:1.7.1
OR			
4.	a. What are the different MOS Layers? Discuss the λ based design rules for layers and transistors.	6	2:2:1.6.1
	b. Calculate the area capacitance values associated with the following structure, having different layers as shown in figure 4.1.	6	3:2:1.7.1

 


Fig 4.1

Note: relative "C" value for polysilicon-to-substrate=0.1 pf x 10⁻⁴/μm² and metal1-to-substrate=0.075 pf x 10⁻⁴/μm².

	c.	Derive the expression for total delay for N stage of NMOS and CMOS inverters by assuming the width factor $f=e$.	8	3:2:1.7.1
Module-3				
5.	a.	Derive the scaling factor for the following parameter 1. Channel resistance. 2. Parasitic capacitance. 3. Gate delay.	6	3:1:1.7.1
	b.	Explain carry select adder with neat block diagram.	6	2:2:1.6.1
	c.	Explain dynamic and Domino logic families with its advantages and disadvantages.	8	2:2:1.6.1
OR				
6.	a.	With truth table explain the operation of 2 input NAND using pseudo nMOS logic.	6	2:2:1.6.1
	b.	With relevant diagram discuss Manchester carry chain operation.	6	2:2:1.6.1
	c.	Explain ALU functions like EX-OR, EX-NOR, AND and OR operations with an adder. Draw the block diagram of 4-bit ALU using adder element.	8	2:2:1.6.1
Module-4				
7.	a.	Explain the following logics 1. clocked CMOS logic 2. n-p CMOS logic	6	2:2:1.6.1
	b.	Draw the block diagram of generic structure of FPGA fabric and explain it.	6	2:4:1.6.1
	c.	Explain parity generator with NMOS implementation with stick diagram.	8	2:2:1.6.1
OR				
8.	a.	Discuss the architectural issues related to VLSI sub system design.	6	2:2:1.6.1
	b.	Explain the goals and techniques of FPGA based system design.	6	2:4:1.6.1
	c.	Explain 4-way data selector (multiplexer) with Boolean expression and nMOS stick diagram.	8	2:2:1.6.1
Module-5				
9.	a.	Explain scan-based design with necessary diagrams.	6	2:5:1.6.1
	b.	What are the requirements for system timing considerations.	6	2:3:1.6.1
	c.	Explain 3 transistor dynamic RAM cell with schematic diagram.	8	2:3:1.6.1
OR				
10	a.	Explain logic verification principles.	6	2:5:1.6.1
	b.	Explain nMOS pseudo static RAM cell with its schematic.	6	2:3:1.6.1
	c.	Explain the following 1. Ad hoc testing 2. BIST	8	2:5:1.6.1

** ** *