

USN

--	--	--	--	--	--	--	--	--

Course Code

2	1	E	C	4	2
---	---	---	---	---	---

Fourth Semester B.E. Degree Examinations, September 2024
NETWORK THEORY AND CONTROL SYSTEMS

Duration: 3 hrs

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
 2. Missing data, if any, may be suitably assumed.

<u>Q. No</u>	<u>Question</u>	<u>Marks</u>	<u>(RBTL:CO:PI)</u>
--------------	-----------------	--------------	---------------------

MODULE – 1

- | | | | |
|----|--|----|-----------------|
| 1. | a. Find the current through $4\ \Omega$ resistor as shown in Fig. 1(a) by using loop current method. | 10 | (3 : 1 : 2.1.3) |
|----|--|----|-----------------|

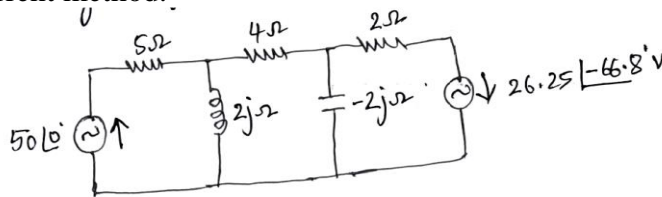


Fig. 1(a)

- | | | | |
|----|---|----|-----------------|
| b. | Use Mesh Analysis, determine what value of V_2 in the network shown in Fig. 1(b) causes the voltage $v = 0$ volts across the $20\ \Omega$ resistor. | 10 | (3 : 1 : 2.1.3) |
|----|---|----|-----------------|

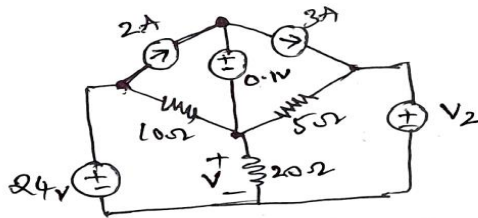


Fig. 1(b)

OR

- | | | | |
|----|---|----|-----------------|
| 2. | a. Find the current in all the resistors by node voltage method as shown in Fig. 2(a). Also write the steps involved in digital simulation. | 10 | (3 : 5 : 5.2.2) |
|----|---|----|-----------------|


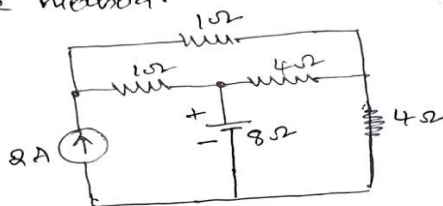


Fig. 1 (c)


- | | | | |
|----|--|----|-----------------|
| b. | Using Millman's theorem find I_L for the network shown in the Fig. 2(a). | 10 | (3 : 5 : 5.2.2) |
|----|--|----|-----------------|

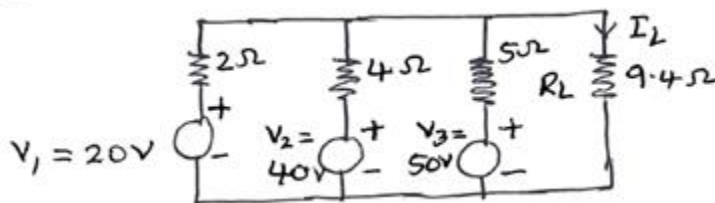

MODULE – 2


- | | | | |
|----|--|----|-----------------|
| 3. | a. Derive the expression for Y-parameters in terms of (i) Z parameters (ii) H-parameters (iii) Transmission Parameters | 10 | (3 : 1 : 2.1.3) |
|----|--|----|-----------------|

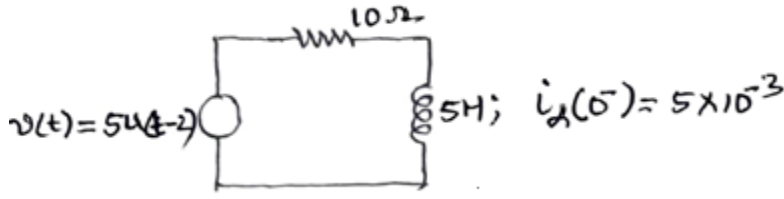- b. Apply the Laplace Transform to obtain the response of current $i(t)$ in the circuit shown in Fig. 3(b). 10 (3 : 1 : 2.1.3)




OR

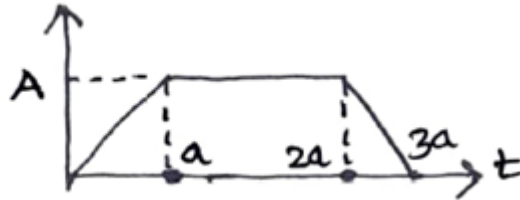4. a. Find the Laplace transform for the wave form shown in Fig. 4 (a). 10 (3 : 1 : 2.1.3)




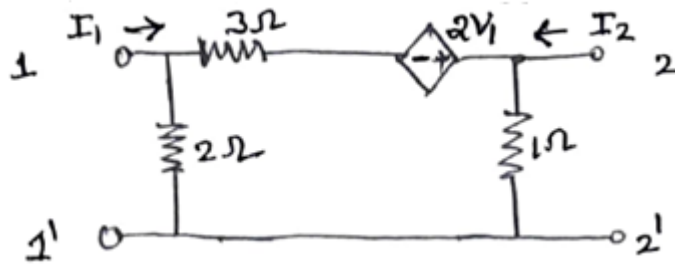- b. Determine Y-parameters for the network shown in the Fig. 4 (b). 10 (3 : 1 : 2.1.3)




MODULE – 3

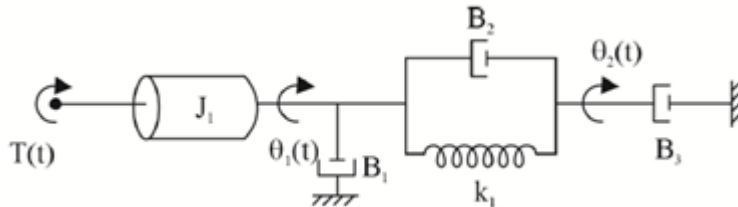5. a. Define control system and explain with an example 10 (3 : 2 : 2.1.3)
 b. For the Rotational system shown in Fig. 5 (b), draw the electrical network based on T-I analogy. 10 (3 : 2 : 2.1.3)



OR

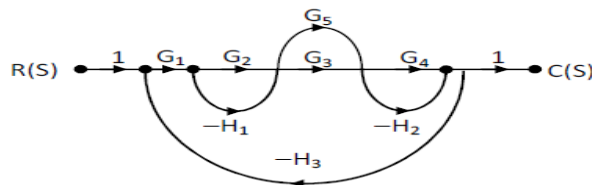6. a. Find Transfer Function for the following signal flow graph shown in Fig. 6 (a). 10 (3 : 2 : 2.1.3)



- b. Define transfer function. Derive an expression for the transfer function of a closed loop negative feedback system. 10 (3 : 2 : 2.1.3)

MODULE – 4

7. a. The characteristic equation is given by $S^4 + 2S^2 + 1 = 0$. 10 (3 : 4 : 2.1.3)
 Use RH criterion to determine (i) Number of roots in LHS of s-plane
 (ii) Number of roots in RHS of s-plane (iii) Number of roots on imaginary axis

- b. A system is given by differential equation $\frac{d^2y}{dt^2} + 4\frac{dy}{dt} + 8y = 8$, where y is output and x is input. Determine all time domain specifications for unit step input. **10** (3 :4 : 2.1.3)

OR

8. a. For a system with characteristic equation $F(S) = S^6 + 3S^5 + 4S^4 + 6S^2 + 3S + 2 = 0$. Examine stability **10** (3 :4 : 2.1.3)
- b. Starting from the output equation $C(t)$ derive expressions for (i) Rise time (t_r) (ii) peak overshoot (M_p) of an under damped second order system subjected to unit step input. **10** (3 :4 : 2.1.3)

MODULE – 5

9. a. Obtain the state model for the system represented by the differential equation $\frac{d^3y(t)}{dt^3} + 6\frac{d^2y(t)}{dt^2} + 11\frac{dy(t)}{dt} + 10y(t) = 3u(t)$. **10** (3 :4 : 2.1.3)
- b. A unity feedback system has $G(S) = \frac{K}{S(S+2)(S+10)}$. Draw Bode plot. **10** (3 :4 : 2.1.3)

OR

10. a. Obtain the state transition matrix for $A = \begin{bmatrix} 0 & -1 \\ 2 & -3 \end{bmatrix}$ **10** (3 :4 : 2.1.3)
- b. Sketch the root locus for open loop transfer function $G(S)H(S) = \frac{K}{S(S+3)(S+5)}$. **10** (3 :4 : 2.1.3)

**** ** ***